

# **DIGITAL SYSTEMS**

## **PRACTICUM 4**



**By:**

**MOHAMMAD FAQIH EZA 'AMMAR**

**NIM: L200183178**

**INFORMATION TECHNOLOGY**

**FACULTY OF COMMUNICATION AND INFORMATICS**

**UNIVERSITY OF MUHAMMADIYAH SURAKARTA**

## Assignment Prak 4

### No 1

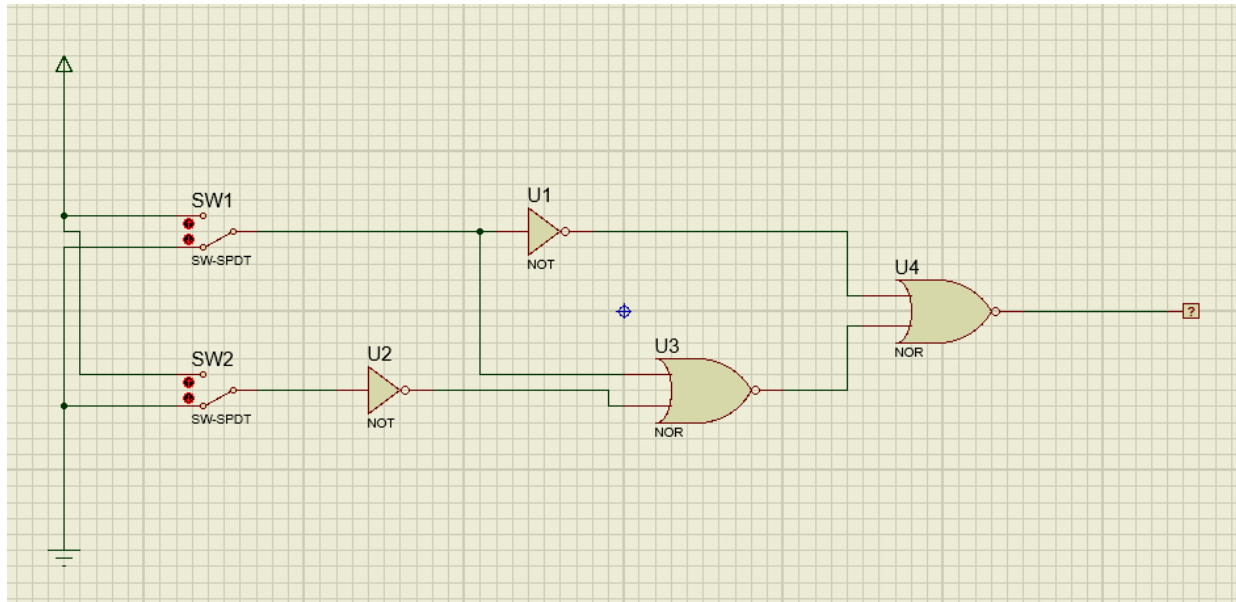


Figure 1.1 – Set of Gate

#### 1. Truth Table

X	Y	F
0	0	0
0	1	0
1	0	1
1	1	1

#### 2. Time Diagram




L1

#### 3. Boolean Function

$$F = \neg(\neg X + \neg(X + \neg Y)) = X(X + \neg Y)$$

## Assignment Prak 4

### No 2

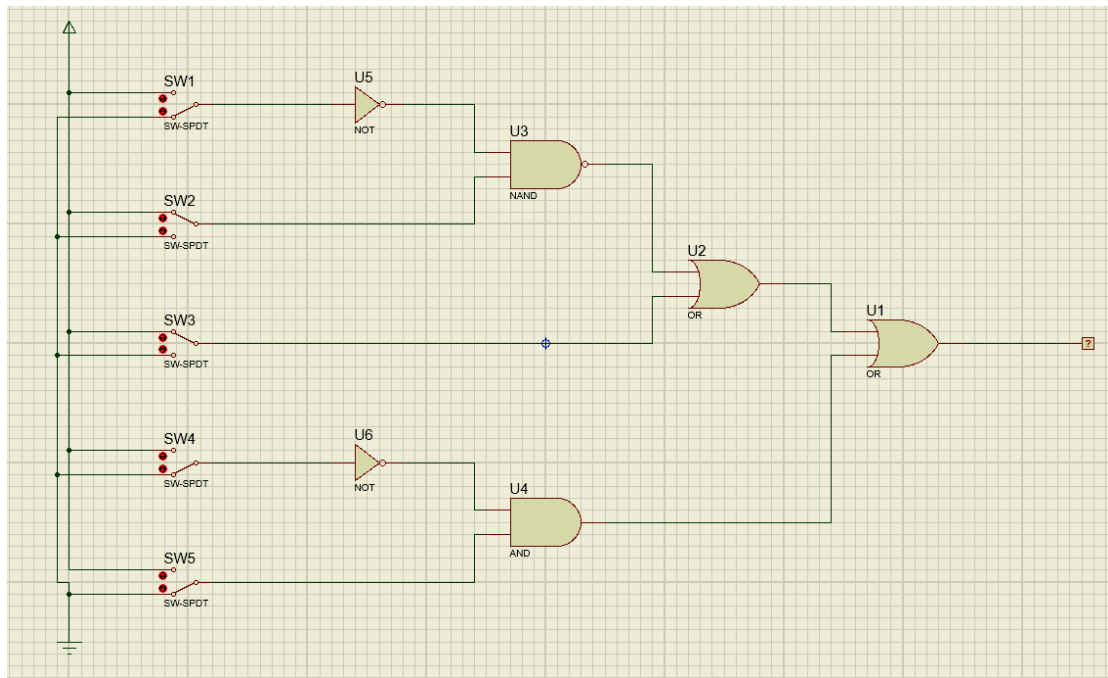

Picture 2.1 - Set of gate for boolean function  $F = (\neg(\neg A.B) + C) + (\neg D.E)$